

Assignment B-4 Exercise 3.1 Project 1 and 2

3. Combinational Logic Circuits

3.3.1 Decoder

- **Exercise 3-1:** draw the circuits by using the logic simulator

- **Project 1**

- Draw the 2-to-4 Decoder (the full logic circuit without any sub-circuit)
 - 1) Use 2 inputs(A0, A1) and 1 enable(Enable), 4 outputs (D0, D1, D2, D3)
 - 2) Draw the full circuits **without** any sub-circuit
 - 3) Show the test results by using testBench
 - 4) Show the test result

Extra points
for the 3x8 Decoder


3. Combinational Logic Circuits

3.3.1 Decoder

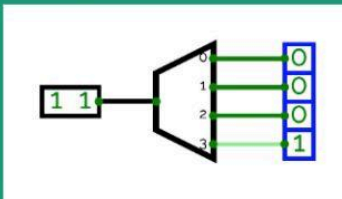
- **Exercise 3-1:**

- **Project 2**

- Use the built-in 2-to-4 Decoder (Decoder or Demultiplexer)
 - Draw the Circuit
 - Add the TestBench
 - Show the Test Result




Using Decoder

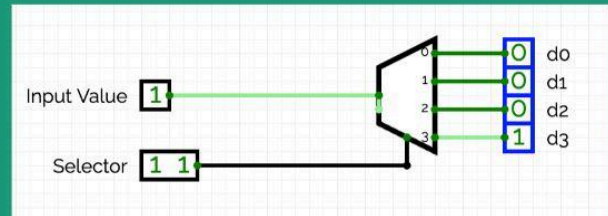

Using DeMux

2x4 Decoder Circuit

1) Design Screenshot

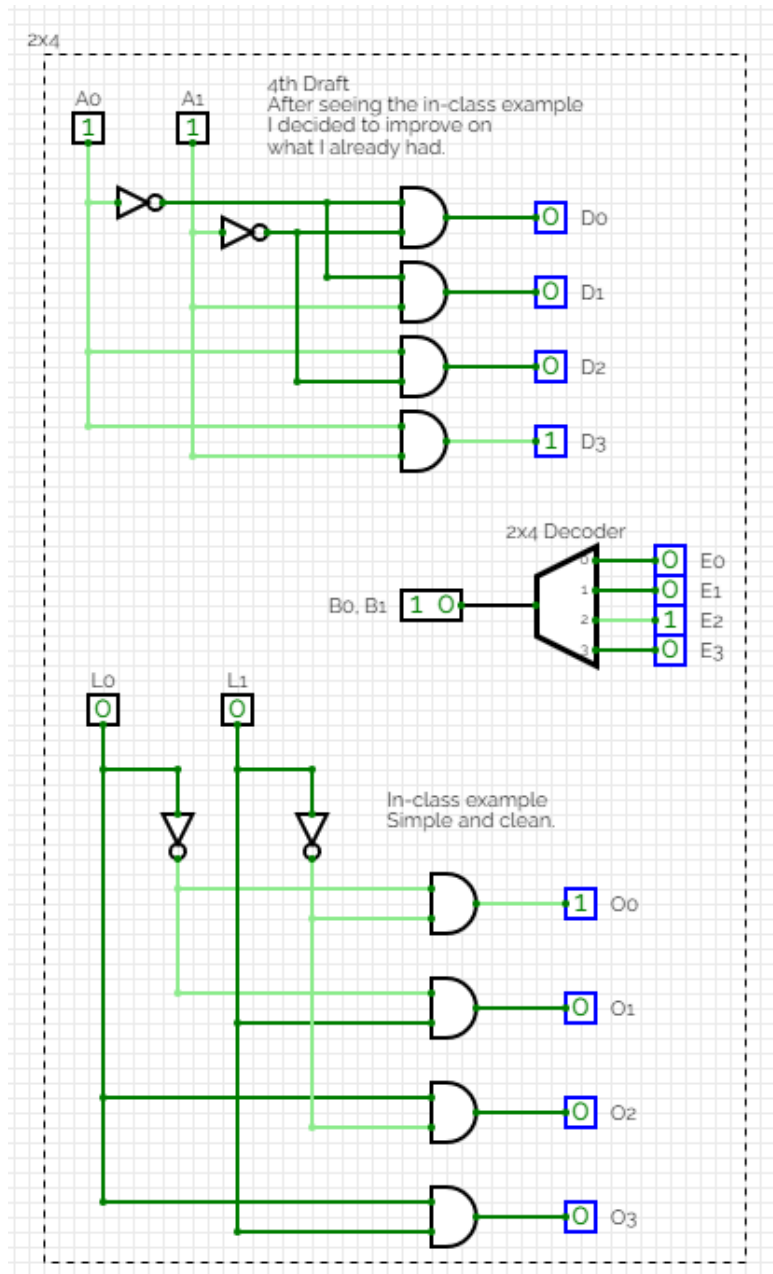

2) Testbenches

Title: 2x4 Test

Sequential Test

Combinational Test

	INPUTS ⊞		OUTPUTS ⊞			
Label	A0	A1	D0	D1	D2	D3
Bitwidth	1	1	1	1	1	1

Group 1

Click + to add tests to the group

0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

+

New Group

Import from CSV

Export as CSV

Attach

Title: 2x4 Decoder Test

Sequential Test

Combinational Test

	INPUTS ⊞	OUTPUTS ⊞			
Label	2x4 Input	E0	E1	E2	E3
Bitwidth	2	1	1	1	1

Group 1

Click + to add tests to the group

00	1	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1

+

New Group

Import from CSV

Export as CSV

Attach

3) Test Results

TESTBENCH

Test: 2x4 Test Type: Combinational

Group: Group 1 Case: 1

LABELS	A0	A1	D0	D1	D2	D3
Bitwidth	1	1	1	1	1	1
Current Case	0	0	1	0	0	0
Result						

4 out of 4 Tests Passed [View Detailed](#)

TESTBENCH

Test: 2x4 Decoder Test Type: Combinational


Group: Group 1 Case: 1

LABELS	2x4 Input	E0	E1	E2	E3
Bitwidth	2	1	1	1	1
Current Case	00	1	0	0	0
Result					

4 out of 4 Tests Passed [View Detailed](#)

3x8 Decoder Circuit

1) Design Screenshot

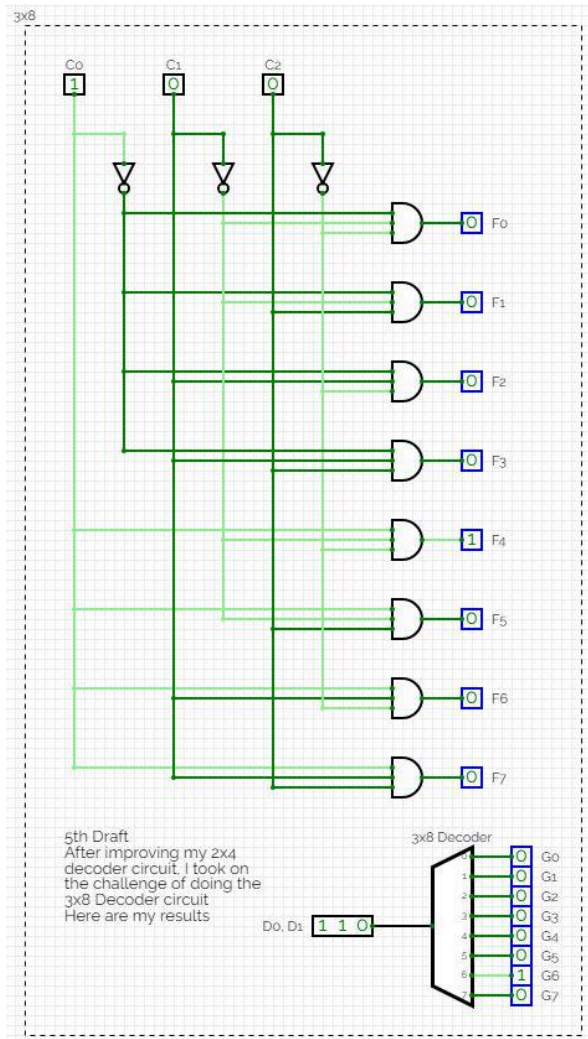

2) Testbenches

Title: 3x8 Test

Sequential Test

Combinational Test

	INPUTS 			OUTPUTS 							
Label	C0	C1	C2	F0	F1	F2	F3	F4	F5	F6	F7
Bitwidth	1	1	1	1	1	1	1	1	1	1	1

Group 1

Click + to add tests to the group

0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0	0
0	1	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	0	1

+

New Group

Import from CSV

Export as CSV

Attach

Title: 3x8 Decoder Test

Sequential Test

Combinational Test

	INPUTS 	OUTPUTS 							
Label	3x8 Input	G0	G1	G2	G3	G4	G5	G6	G7
Bitwidth	3	1	1	1	1	1	1	1	1

Group 1

Click + to add tests to the group

000	1	0	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0	0
011	0	0	0	1	0	0	0	0	0
100	0	0	0	0	1	0	0	0	0
101	0	0	0	0	0	1	0	0	0
110	0	0	0	0	0	0	1	0	0
111	0	0	0	0	0	0	0	1	0

+

New Group

Import from CSV

Export as CSV

Attach

3) Test Results

TESTBENCH

Test: 3x8 Test **Type:** Combinational

Edit

Remove

Group:

< Group 1 >

Case:

< 1 >

LABELS	C0	C1	C2	F0	F1	F2	F3
Bitwidth	1	1	1	1	1	1	1
Current Case	0	0	0	1	0	0	0
Result	<div><div></div></div>						

Validate

Run All

8 out of 8 Tests Passed [View Detailed](#)

TESTBENCH

Test: 3x8 Decoder Test **Type:** Combinational

Edit

Remove

Group:

< Group 1 >

Case:

< 1 >

LABELS	3x8 Input	G0	G1	G2	G3	G4
Bitwidth	3	1	1	1	1	1
Current Case	000	1	0	0	0	0
Result	<div><div></div></div>					

Validate

Run All

8 out of 8 Tests Passed [View Detailed](#)

