

Assignment B-5 Exercise 3.2 Project 1 and 2

3.3.2 Multiplexer

- Exercise 3-2:

- Project 1

- 1) Draw the 4x1 multiplexer using the circuit simulator(Circuitverse, Digital)
- 2) Show the truth tables and test results by using the simulation tool


- Project 2

- 1) Draw 8x1 multiplexer by using your sub-circuit 2x1 mux
 - 4 2x1 Mux + 1 4x1 Mux
- 2) Show the test results and truth table


2 tries with different combos to show that it works just like a multiplexer

Project 1

1) Design Screenshot

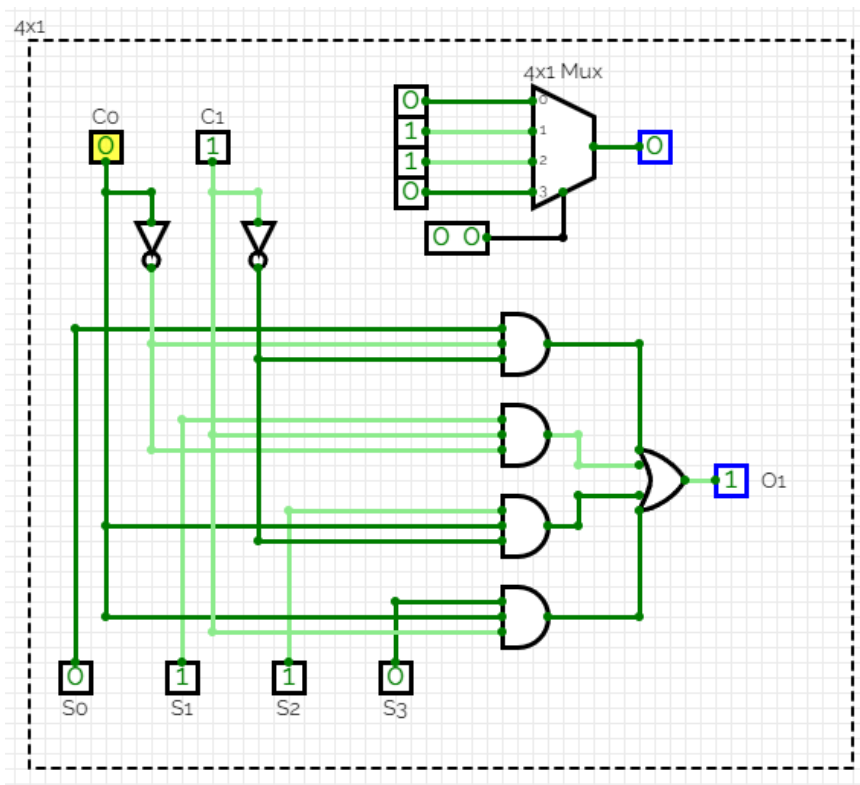

Part 1

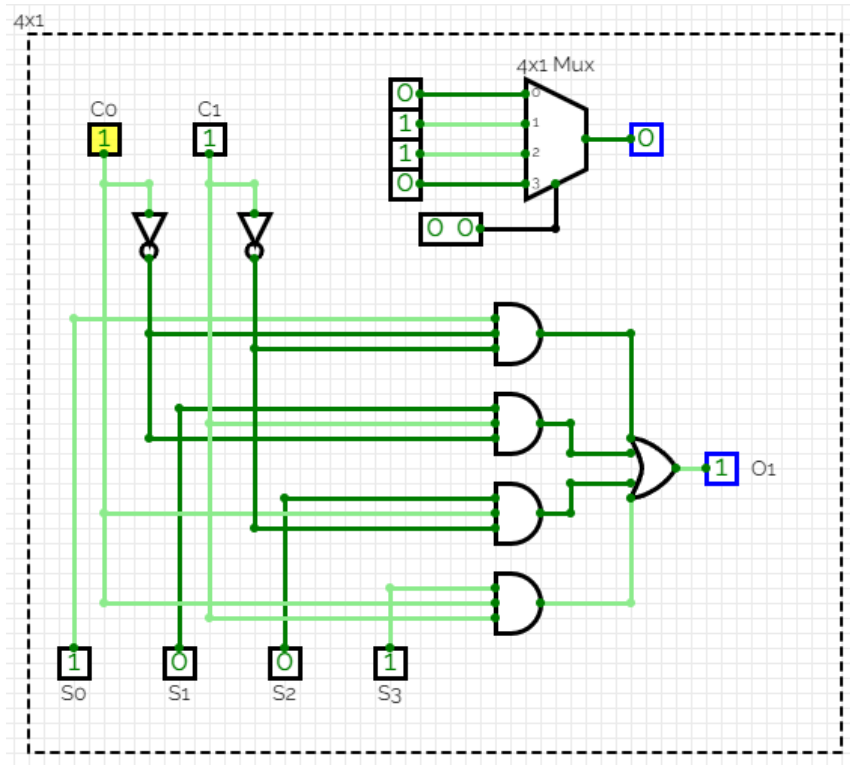

Part 2

2) Testbench

Title:

Sequential Test ☐ Combinational Test ☒

	INPUTS <input type="checkbox"/>		OUTPUTS <input type="checkbox"/>
Label	C0	C1	O1
Bitwidth	1	1	1

Group 1

Click + to add tests to the group

0	0	0
0	1	1
1	0	1
1	1	0

New Group

Title: 4x1 Test pt.2

Sequential Test

Combinational Test

	INPUTS +		OUTPUTS +
Label	C0	C1	O1
Bitwidth	1	1	1

Group 1

Click + to add tests to the group

0	0	1
0	1	0
1	0	0
1	1	1

+

New Group

Import from CSV

Export as CSV

Attach

3) Test Result

TESTBENCH ▾

Test: 4x1 Test pt.1

Type: Combinational

Edit

Remove

Group: < Group 1 >

Case: < 1 >

LABELS	C0	C1	O1
Bitwidth	1	1	1
Current Case	0	0	0
Result			

Validate

Run All

4 out of 4 Tests Passed [View Detailed](#)

TESTBENCH

Test: 4x1 Test pt.2

Type: Combinational

Edit

Remove

Group: < Group 1 >

Case: < 1 >

LABELS	C0	C1	O1
Bitwidth	1	1	1
Current Case	0	0	1
Result			


Validate


Run All

4 out of 4 Tests Passed [View Detailed](#)

Project 2

1) Design Screenshot

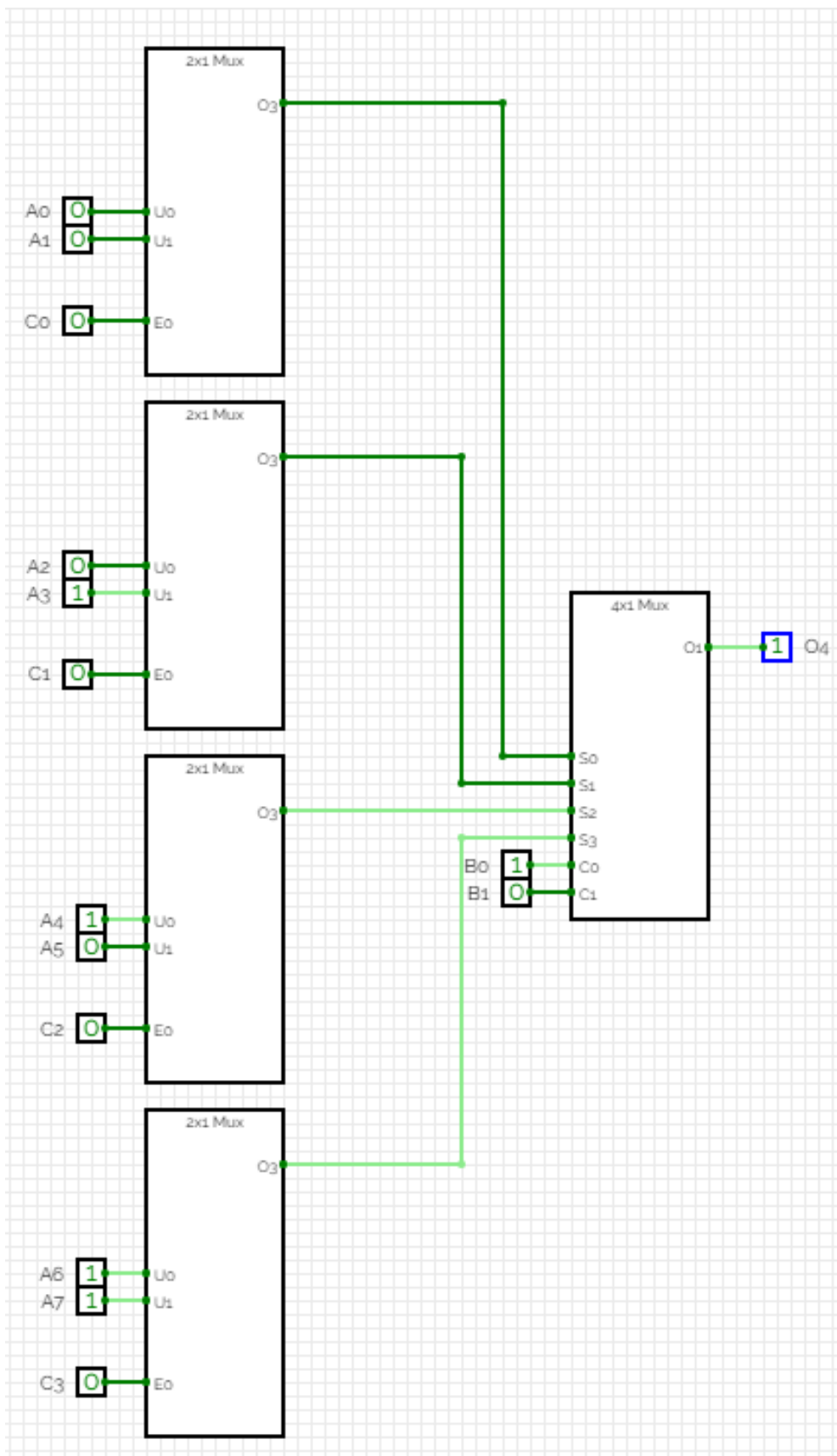

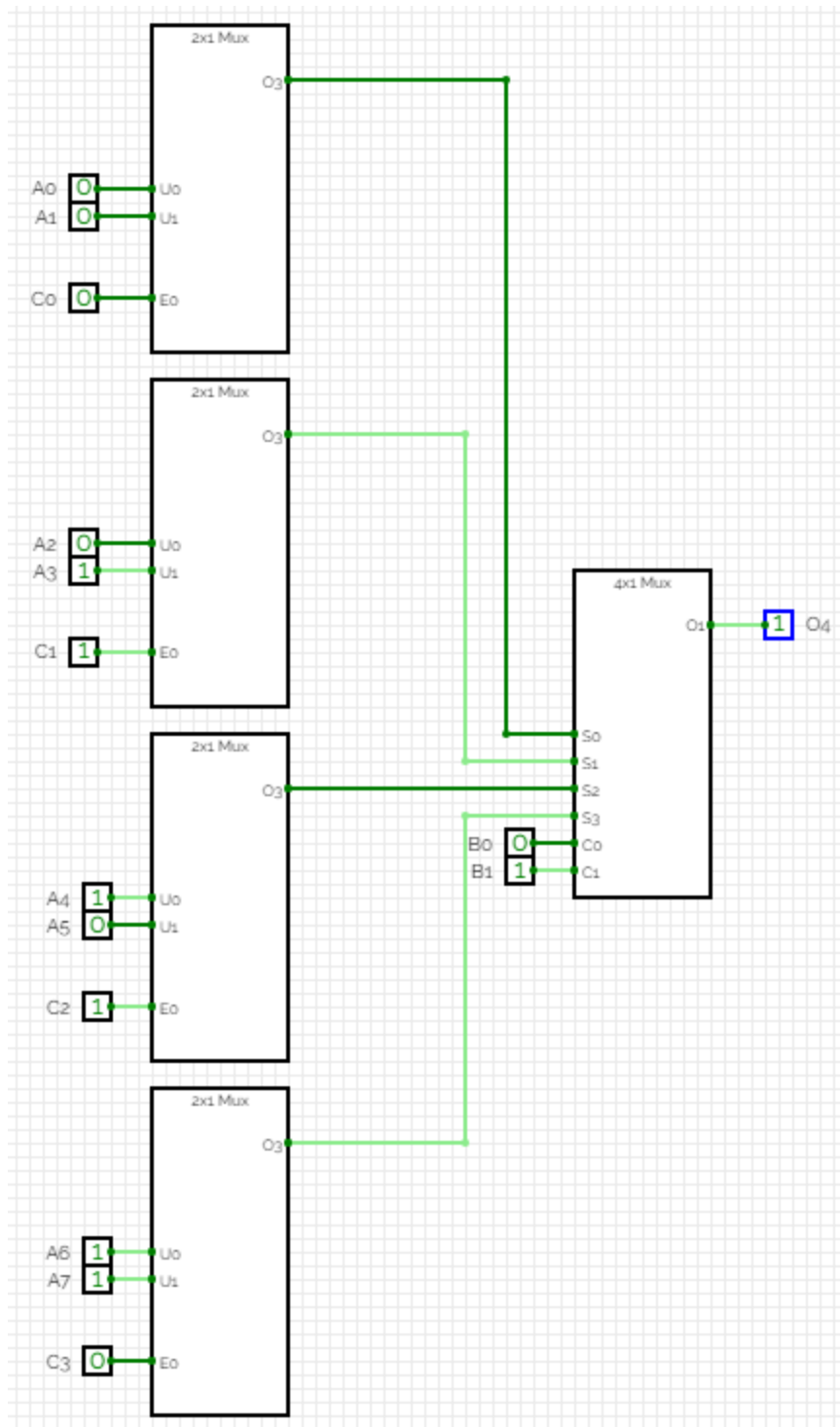

Part 2

2) Testbench

Title:8x1 Test Pt.1

Sequential Test

Combinational Test

	INPUTS <div></div>								OUTPUTS <div></div>
Label	A0	A1	A2	A3	A4	A5	A6	A7	O4
Bitwidth	1	1	1	1	1	1	1	1	1

Group 1

Click + to add tests to the group

0	0	0	0	0	0	0	0	0
0	1	0	1	0	1	0	1	0
1	0	1	0	1	0	1	0	1
1	1	1	1	1	1	1	1	1

+

New Group

Import from CSV

Export as CSV

Attach

Title:8x1 Test Pt.2

Sequential Test

Combinational Test

	INPUTS <div></div>								OUTPUTS <div></div>
Label	A0	A1	A2	A3	A4	A5	A6	A7	O4
Bitwidth	1	1	1	1	1	1	1	1	1

Group 1

Click + to add tests to the group

0	0	0	0	0	0	0	0	0
0	1	0	1	0	1	0	1	1
1	0	1	0	1	0	1	0	0
1	1	1	1	1	1	1	1	1

+

New Group

Import from CSV

Export as CSV

Attach

3) Test Result


TESTBENCH

Test: 8x1 Test Pt.1

Type: Combinational


Edit

Remove

Group:  Group 1 

Case:  1 

LABELS	A0	A1	A2	A3	A4	A5	A6
Bitwidth	1	1	1	1	1	1	1
Current Case	0	0	0	0	0	0	0
Result							

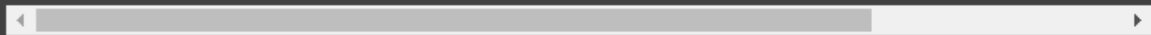

Validate

Run All

4 out of 4 Tests Passed [View Detailed](#)



TESTBENCH

Test: 8x1 Test Pt.2

Type: Combinational


Edit

Remove

Group:  Group 1 

Case:  1 

LABELS	A0	A1	A2	A3	A4	A5	A6
Bitwidth	1	1	1	1	1	1	1
Current Case	0	0	0	0	0	0	0
Result							

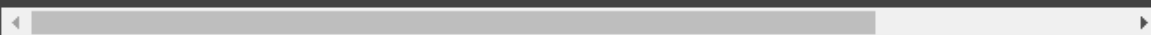


Validate

Run All

4 out of 4 Tests Passed [View Detailed](#)

Extra:

8x1

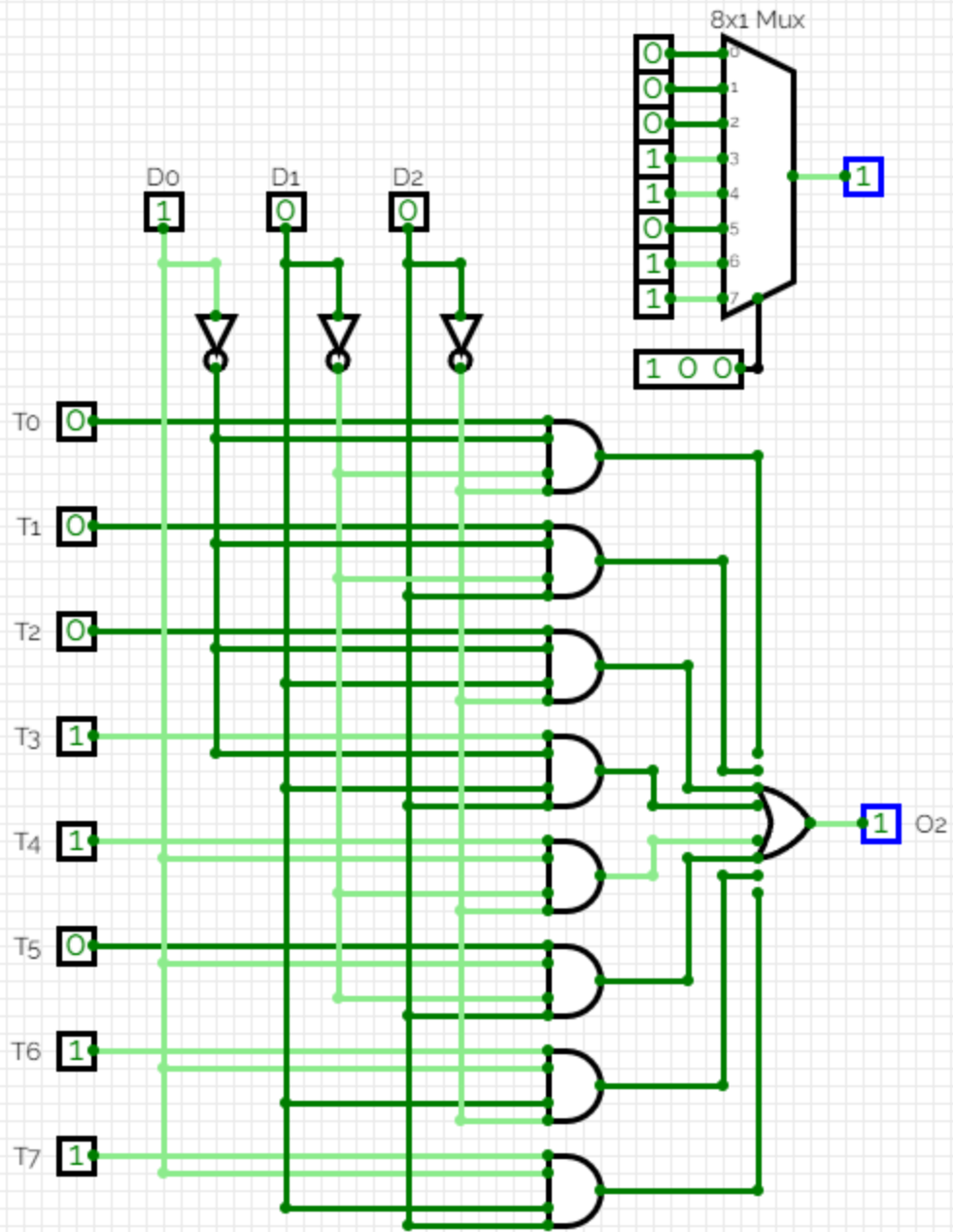

8x1 Mux

