

Assignment B-6 Exercise 3.3 $F(A,B,C) = \Sigma(1,3,5,6)$

• Exercise 3-3:

• Implementing the Boolean function with MUX

- $F(A, B, C) = \Sigma(1,3,5,6)$
- The function is the same as previous example
 - Take the B and C as the selection input
 - Take the A as the input of 4x1 MUX


- Draw the MUX circuit
 - for this Boolean function

	BC			
	00	01	10	11
A	0			
	1			
F				

Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1) Design Screenshot

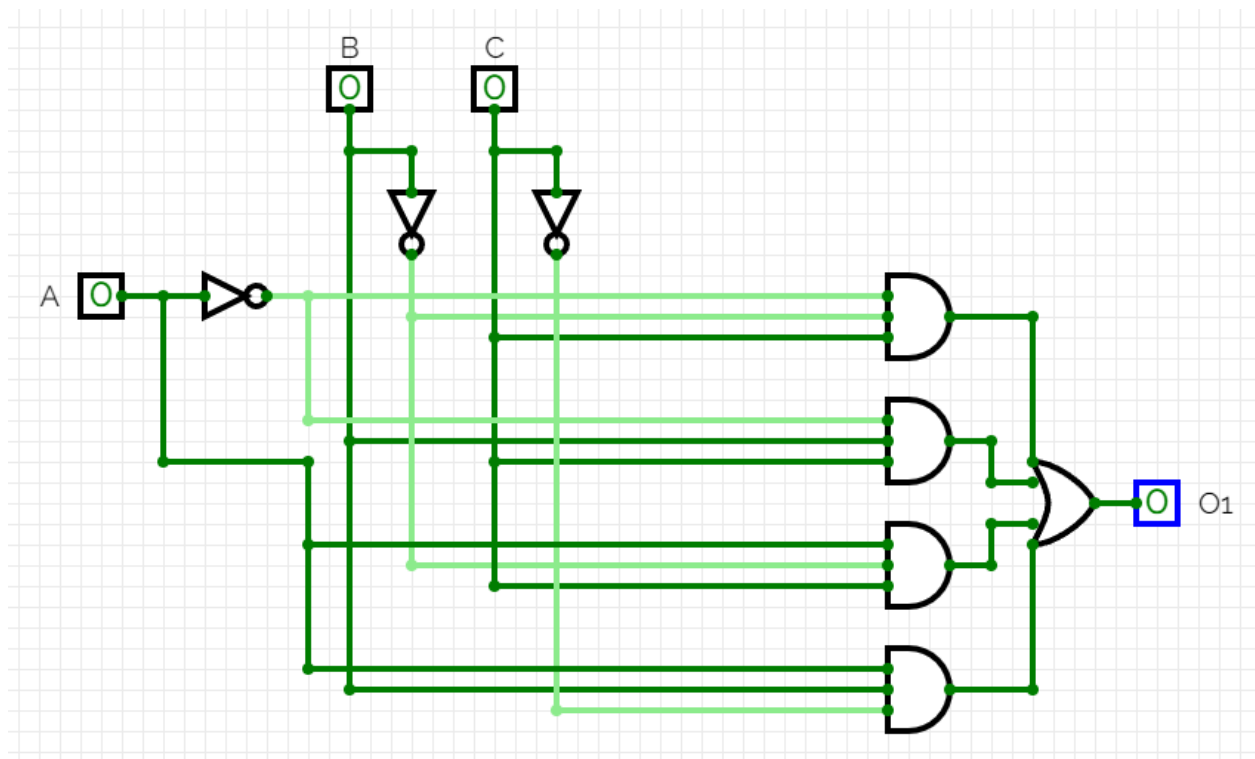

Don't know if I'm allowed to turn A from 4 inputs to just 1. But I did it cause it seems more efficient/cleaner.

2) Testbench

Title:

Sequential Test Combinational Test

	INPUTS <input type="checkbox"/>			OUTPUTS <input type="checkbox"/>
Label	A	B	C	O1
Bitwidth	1	1	1	1

Group 1

Click + to add tests to the group

0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

+ New Group

Import from CSV Export as CSV Attach

3) Test Result

TESTBENCH ☐

Test: Test1 **Type:** Combinational

Edit

Remove

Group: Group 1

Case: 1

LABELS	A	B	C	O1
Bitwidth	1	1	1	1
Current Case	0	0	0	0
Result				

Validate

Run All

8 out of 8 Tests Passed [View Detailed](#)